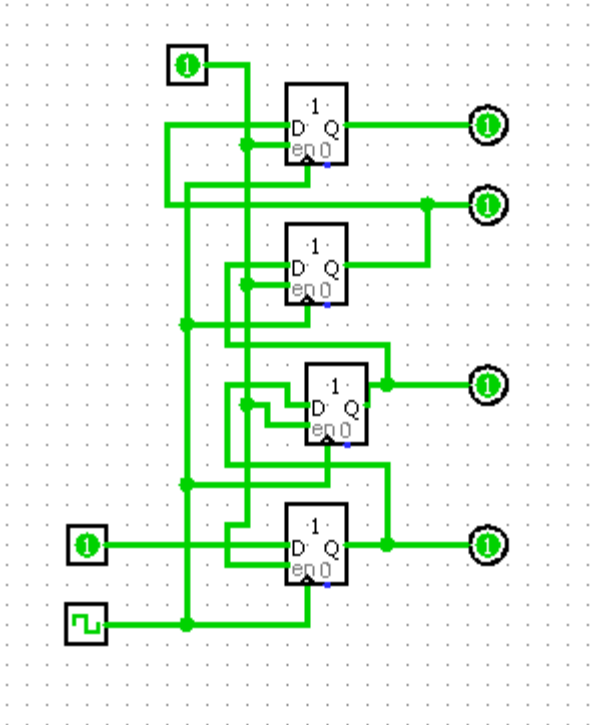


Q1: Simulate a 8 bit shift register using logic-sim. A 4 bit shift register design is shown.



(10 Points)

Q2: Study 7495 data sheet, and implement serial in and serial out shift register. Test using LEDs



7495 (4-bit shift register, parallel in, parallel out, serial input)

(15 Points)

Q3: Simulate the multi-function Shift register using logic-sim

## Functions:

s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	(unused - let's load 0s)

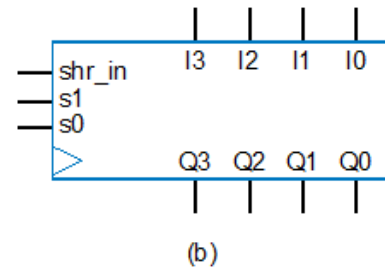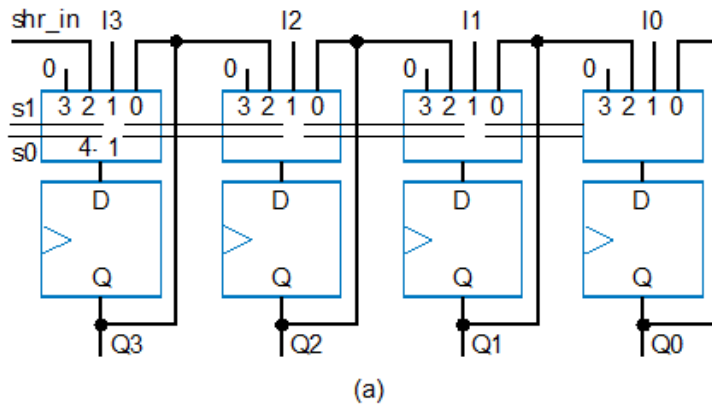

(15 Points)

Q4: Study 74194 (4-bit bidirectional universal shift register)

Test each of the functionality by applying appropriate test data and test output using LEDs/  
Seven segment displays.

(25Points)

Q5:

Simulate a 4 bit Counter using JK flip flops ( Logic-sim) .

(10Points)

**Logic-sim simulation submission should be individual.** Course work submission through

Email: [cs225.iitp@gmail.com](mailto:cs225.iitp@gmail.com)

(use email subject Lab9\_Logicsim\_your roll number).

This work should be completed in Lab.