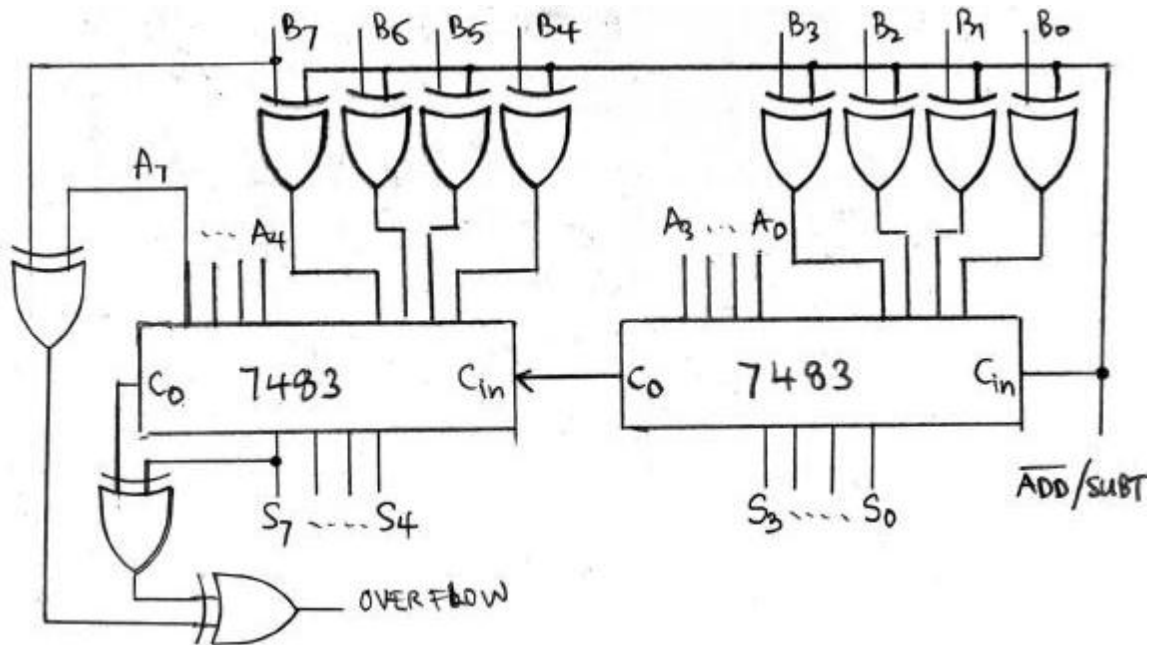


1. To implement a binary full-adder with a dual 4-to-1-line multiplexer and a single inverter.

(10 points)

2. Study 7483 and design an 8-bit adder/subtractor with overflow detection using 7483s.



(40 points)